

Sequential Logic Design


Lecture 5

Outline

- Create scalar and wide combinatorial circuits using gate-level, dataflow, and behavioral modeling
- Write models to read switches and push buttons, and output on LEDs
- Simulate and understand the design output
- Synthesize, implement and generate bitstreams
- Download bitstreams into the board and verify functionality

Verilog HDL

Three kinds of modeling styles

 

Gate-Level Modeling

Built-in primitive gates modeling are supported

Multiple-input (one output)

and | **nand** | **or** | **nor** | **xor** | **xnor** [instance name] (out, in1, ..., inN);

Multiple-output (one input)

buf | **not** [instance name] (out1, out2, ..., out2, input);

Tristate (one input, one control signal, one output)

bufif0 | **bufif1** | **notif0** | **notif1** [instance name] (outputA, inputB, controlC);

Pull gates (single output, no input)

pullup | **pulldown** [instance name] (output A);

// [] is optional and | is selection

Multiple Instances of the Same Type of Gate in One Construct

and [inst1] (out11, in11, in12), [inst2] (out21, in21, in22, in23), [inst3] (out31, in31, in32, in33);

Allowing the delays to be expressed when instantiating gates

and #5 A1(out1, in1, in2); // the rise and fall delays are 5 units

and #(2,5) A2(out2, in1, in2); // the rise delay is 2 units and the fall delay is 5 units

notif1 #(2, 5, 4) A3(out3, in2, ctrl1); //the rise delay is 2, fall delay is 5, turn-off delay is 4 units

Dataflow Modeling

- Mainly used to describe combinational circuits.
- The basic mechanism used is the **continuous assignment**.
- In a continuous assignment, a value is assigned to a data type called **net**.
- The syntax of a continuous assignment is:
`assign [delay] LHS_net = RHS_expression;`

The statement is evaluated at any time any of the source operand value changes and the result is assigned to the destination net after the delay unit.

```
assign out1 = in1 & in2; // perform and function on in1 and in2 and assign the result to out1
assign out2 = not in1;
assign #2 z[0] = ~(ABAR & BBAR & EN); // perform function and assign the result after 2 units
```

Target in the Continuous Assignment Expression

1. A scalar net

```
assign out1 = in1 & in2;
```

2. Vector net

3. Constant bit-select of a vector

```
assign #2 z[0] = ~(ABAR & BBAR & EN);
```

4. Constant part-select of a vector

5. Concatenation of any of the above

```
wire COUT, CIN; // scalar net declaration
```

```
wire [3:0] SUM, A, B; // vector nets declaration
```

```
assign {COUT,SUM} = A + B + CIN; // A and B vectors are added with CIN and the result is
```

```
// assigned to a concatenated vector of a scalar and vector nets
```

Note: multiple continuous assignment statements are not allowed on the same destination net.

Behavioral Modeling

- Used to describe complex circuits, primarily sequential circuits, but also pure combinatorial circuits.
- The statements for modeling the behavior of a design are:
`initial [timing_control] procedural_statements; //both may contain multiple procedural statements`
`always [timing_control] procedural_statements;`
- They are executed concurrently, Both **initial** and **always** statements are executed at time=0 and then only **always** statements are executed during the rest of the time
- The **initial** statement is **non-synthesizable** and is normally used in testbenches
- The **always** statement is **synthesizable**

Numbers Representation

`[size]'``[signed]``[radix]``value` ([] indicates optional)

size The number of binary bits the number is comprised of Default is 32 bits.

' A separator

signed including S Indicates if the value is signed Default is unsigned.

Radix b : binary, o : octal, h : hex, d : decimal (also default)

Note: X represents unknown, Z represents high impedance
(none of the above is case dependent)

Number Representation

In Verilog HDL a **signal** can have the following four basic values:

- i. 0 : logic-0 or false
- ii. 1 : logic-1 or true
- iii. x : unknown
- iv. z : high-impedance

Integer numbers can be written in

- i. simple decimal or
i.e. 16, -34

- ii. base format

[size] 'base value

number of bits ← [size] ↓ base → Unsigned sequence of digits valid for the specified base
o (octal), b (binary), d (decimal), h (hexadecimal)

```
wire [4:0] 5'O37 // 5-bit octal representation
```

```
reg [3:0] 4'B1x_01 // 4-bit binary
```

Three types of **constants** in Verilog HDL:

- i. Integer
- ii. Real
- iii. String

Note:

- If the size specified is larger than the value for the specified constant,
 - the number is padded to the left with 0's
 - for the case where the left most bit is x or z then the padding is done with x or z.
- If the size specified is smaller then the extra left most bits are ignored.
- If the size is not specified then it will use 32-bit data.

Procedural Statements

A module may contain an arbitrary number of **initial** or **always** statements and may contain one or more **procedural statements** within them. Procedural statements are executed sequentially

Procedural Assignment

[delay] register_name = [delay] expression; // blocking

[delay] register_name <= [delay] expression; // non-blocking

Example- Procedural Assignment:

// time 0: a=0; time 10: a=1; time 15 (#10+#5): a=2;

begin

a = 0;

#10 a = 1;

#5 a = 2;

end

// time 0: a=0; time 5: a=2; time 10: a=1;

begin

a <= 0;

#10 a <= 1;

#5 a <= 2;

end

// both assignments are evaluated before a or b changes

begin

a <= b;

b <= a;

end

Conditional Statement

condition ? Expression1 : expression2;

Example- modeling tri-state buffer:

assign data_out = (enable) ? data_reg : 8'bz;

Example

(a) ? 4'b110x : 4'b1000;

	0	1	x	z
0	0	x	x	x
1	x	1	x	x
x	x	x	x	x
z	x	x	x	x

- If one of the expressions is of real type then the result of the whole expression should be 0 (zero).
- If expressions have different lengths, then length of an entire expression will be extended to the length of the longer expression.
- Trailing 0s will be added to the shorter expression.
- The conditional operator can be nested and its behavior is identical with the case statement behavior

Case Statements

```
case (  
<case1>: <statement>;  
<case1>: <statement>;  
....  
default : <statement>
```

loop Statements

Forever, repeat, while, for

Wait Statements

Example

```
case (i)  
0 : y = a;  
1 : y = b;  
2 : y = c;  
default :$display("Error");  
endcase
```

A Multiplexer - Two Ways

```
reg [4:0] mux;  
reg [1:0] addr;
```

```
mux = (addr == 2'b00) ? i0 :  
      ((addr == 2'b01) ? i1 :  
      ((addr == 2'b10) ? i2 :  
      ((addr == 2'b11) ? i3 :  
      4'bz)));
```

```
case (addr)  
  2'b00: mux = i0;  
  2'b01: mux = i1;  
  2'b10: mux = i2;  
  2'b11: mux = i3;  
  default: mux = 4'bz;  
endcase
```

To generate a combinatorial circuit, the **always** block

- (i) should not be edge sensitive,
- (ii) every branch of the conditional statement should define all output, and
- (iii) every case of case statement should define all output and must have a default case.

The destination (LHS) should be of **reg** type; either scalar or vector

```
reg m; // scalar reg type
```

```
reg [7:0] switches; // vector reg type
```

Example 2-to-1 Mux

```
always @ (x or y or s) //The sensitive list, always block executes when changed
begin
    if(s==0)
        m=y;
    else
        m=x;
end
```

Lab 2

- 1. Create a two-bit wide 2-to-1 multiplexer using gate-level modeling.**
 - a. Synthesize the design.
 - b. Implement the design.
 - c. Generate the bitstream, download it into the ZedBoard to verify the functionality.
- 2. Model a two-bit wide 2-to-1 multiplexer using dataflow modeling with net delays of 3 ns.**
 - a. Simulate the design for 100 ns and analyze the output. Refer to last slide for the testbench
 - b. Synthesize the design.
 - c. Implement the design.
 - d. Generate the bitstream, download it into the ZedBoard, and verify the functionality.
- 3. Create a two-bit wide 2-to-1 multiplexer using behavioral modeling.**
 - a. Synthesize the design.
 - b. Implement the design.
 - c. Generate the bitstream, download it into the ZedBoard to verify the functionality.
- 4. Create a two-bit wide 3-to-2 multiplexer using two 2-1 multiplexers from parts 1, 2, 3, or 4**
 - a. Synthesize the design.
 - b. Implement the design.
 - c. Generate the bitstream, download it into the ZedBoard to verify the functionality.

Use the following testbench for Lab 2 Part 2.a:


```
initial
begin
  x = 0; y = 0; s = 0;
  #10 x = 1;
  #10 y = 1;
  #10 x = 3; y = 0;
  #10 x = 2; y = 3;
  #10 s = 1;
  #10 x = 1;
  #10 y = 1;
  #10 x = 3; y = 0;
  #10 x = 2; y = 3;
  #20;
end
end
```

Where **x** and **y** are the 2-bit inputs and **s** is the select input

Addition- Ripple Carry Adder

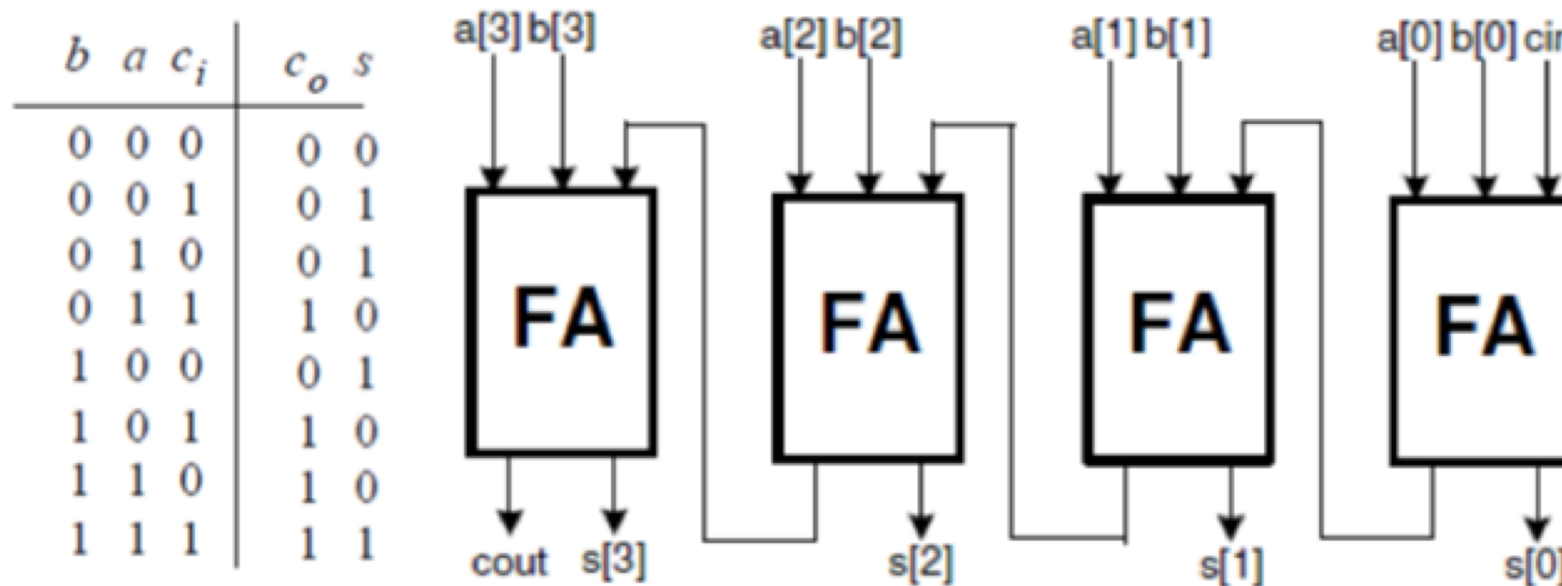5. Create a 4-bit ripple carry adder using dataflow modeling

- Create and add a Verilog module with three one-bit wide inputs (a , b , cin) and one-bit wide two outputs (s and $cout$)
- Simulate the design for 80 ns using the provided testbench and verify that the design works
- Create a 4-bit adder by instantiating the adder created in part 5-a.
- Create the XDC file reflecting the LEDs and Switches of your choice for implementation.
- Synthesize, implement the design, generate the bitstream and download it into the ZedBoard to verify the functionality.



Full Adder Dataflow Testbench

```
reg a, b, cin;
wire cout, s;


fulladder_dataflow DUT (.a(a), .b(b), .cin(cin), .cout(cout), .s(s));

initial
begin
    a = 0; b = 0; cin = 0;
    #10 a = 1;
    #10 b = 1; a = 0;
    #10 a = 1;
    #10 cin = 1; a = 0; b = 0;
    #10 a = 1;
    #10 b = 1; a = 0;
    #10 a = 1;
    #10;
end
```

Carry Lookahead Adder

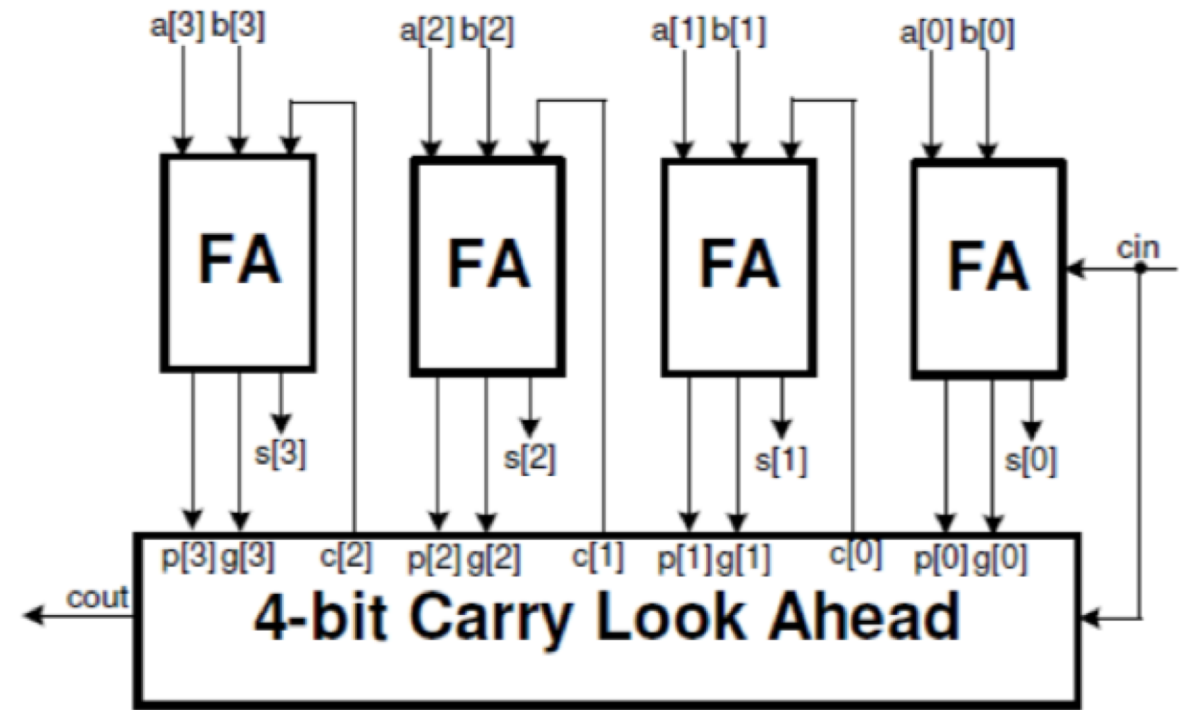6. Create a 4-bit carry Lookahead adder using dataflow modeling

- Modify the ripple carry adder as necessary
- Create the XDC file reflecting the LEDs and Switches of your choice for implementation.
- Synthesize and implement the design.
- generate the bitstream and download it into the ZedBoard to verify the functionality.



Where:

$$P_i = A_i + B_i$$

$$G_i = A_i B_i$$

$$C_{i+1} = G_i + P_i C_i$$